

DPP No. # 05


1. Point P is at instantaneous rest,

$$\epsilon_1 = |v_P - v_A| = \frac{1}{2} B\omega \left(\frac{\ell}{2} + \frac{v}{\omega} \right)^2$$

$$\epsilon_2 = |v_P - v_B| = \frac{1}{2} B\omega \left(\frac{\ell}{2} - \frac{v}{\omega} \right)^2$$

$$|v_A - v_B| = \epsilon_1 - \epsilon_2$$

$$|v_A - v_B| = B\ell v$$

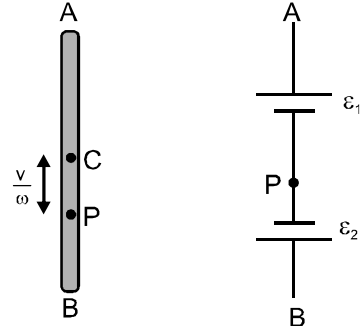


2. $\frac{X_L}{R} = \sqrt{3} \Rightarrow X_L = R\sqrt{3}$

$$i = \frac{100}{\sqrt{(10\sqrt{3})^2 + (10)^2}} = 5A$$

$$L = \frac{10\sqrt{3}}{100\pi} = \frac{\sqrt{3}}{10\pi} H$$

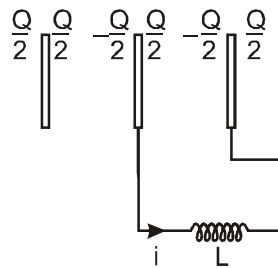3. $\left(\frac{Q}{2} \right)^2 = \frac{1}{2} Li_0^2$

$$\Rightarrow i_0 = \frac{Q}{2\sqrt{LC}}$$




4. impedance $z = \sqrt{(8-2)^2 + (8)^2} = 10 \Omega$


current lags voltage by 37° , then

$$i = \frac{10}{10} \sin(50\pi t - 37^\circ)$$
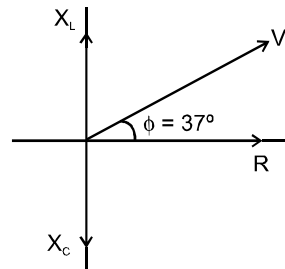
$$V_{AB} = i \times R = 8 \sin(50\pi t - 37^\circ)$$




5.

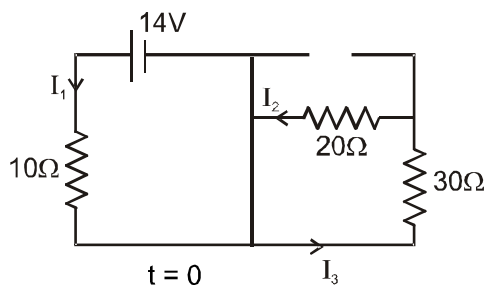

$$I_1 = \frac{14}{10} = 1.4$$

$$I_2 = I_3 = 0$$

6.

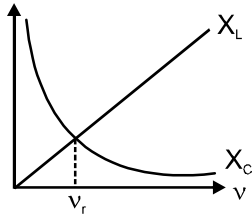

From graph, When frequency is increased more than resonating frequency ($X_C \sim X_L$) will increase hence impedance of the circuit will increase

7.


Only for resonating frequency circuit is able to drive appreciable current. So we can use these type of circuit in tuning of radio and TV for selecting particular frequency sent by a particular source.

8.


$$V_L = 8V, V_R = 6V, V = \sqrt{V_L^2 + V_R^2} = 10 V$$

$$\text{power factor} = \cos \phi = \frac{V_R}{V} = \frac{6}{10} = 0.6$$

9.

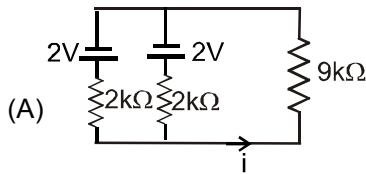

$$i = \frac{2}{9+1} = 0.2 A$$

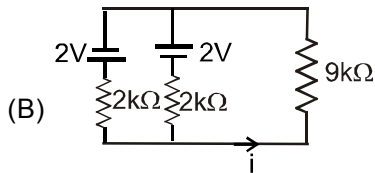

$$i = 0$$


10.

$$\text{Fringe width} = n \frac{\lambda D}{d}$$

From given situation


$$F.W. = \frac{d}{2}$$
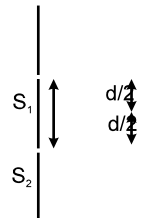
$$\Rightarrow n \frac{\lambda D}{d} = \frac{d}{2} \Rightarrow \lambda = \frac{d^2}{2nD}$$



Hence (C) is possible.

11.

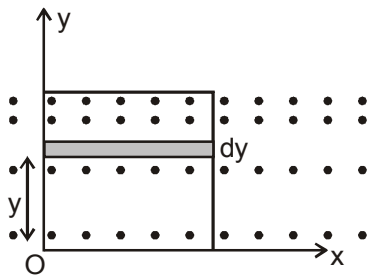

$$\phi = \int \vec{B} \cdot d\vec{A}$$

$$\phi = \int cy^3 t^2 a dy$$

$$\phi = ct^2 a \int_0^a y^3 dy$$

$$\phi = ct^2 a \cdot \frac{a^4}{4}$$

$$\phi = \frac{ct^2 a^5}{4}$$

$$e = \left| -\frac{d\phi}{dt} \right|$$

Now induced e.m.f.

$$e = \left| -\frac{2cta^5}{4} \right| = \frac{2cta^5}{4} = \frac{cta^5}{2}$$

12. For 100th maximum
 $d \sin \theta = 100 \lambda$

$$\sin \theta = \frac{100 \times 5000 \times 10^{-9}}{1 \times 10^{-3}} = \frac{5 \times 10^{-4}}{10^{-3}} = 0.5 = \frac{1}{2}$$

$$\therefore y = D \tan \theta$$

$$= 1 \times \tan 30$$

$$= \frac{1}{\sqrt{3}} = \frac{\sqrt{3}}{3} = \frac{1.732}{3} = 0.577$$

13. The area vector of loop $\vec{A} = \pm \ell b \hat{k}$


$$\& \quad \vec{B} = 20t \hat{i} + 10 t^2 \hat{j} + 50 \hat{k}$$

$$\therefore \text{Magnetic flux is } \phi = \vec{B} \cdot \vec{A} = \pm 50 \ell b$$

$$\therefore \text{emf} = \frac{d\phi}{dt} = 0$$



14.

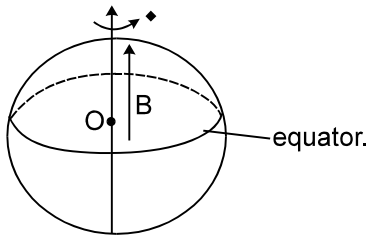

the equator can be seen as a conducting ring of radius R_e revolving with angular velocity ω in a perpendicular magnetic field B .

$$\therefore \text{Potential difference across its center and periphery} = \frac{B\omega R_e^2}{2}$$

Potential at pole = potential of the axis of earth i.e. potential at point O

$$\therefore V_{\text{equator}} - V_{\text{pole}} = \frac{B\omega R_e^2}{2}$$

$$15. \quad \frac{dq}{dt} = i = 0 \quad Q \rightarrow \max$$

$$E_c = \frac{Q^2}{2C} \Rightarrow \max$$

$$E_L = \frac{Li^2}{2} \Rightarrow \text{zero}$$

16. Let at time t the angle between magnetic field and area vector (semicircle) be θ , then $\theta = \omega t$

$$\phi = \vec{B} \cdot \vec{S} = \frac{\pi a^2 B}{2} \cos \omega t$$

$$\varepsilon = -\frac{d\phi}{dt} = \frac{\pi B a^2 \omega}{2} \sin \omega t$$

$$\varepsilon_0 = \frac{\pi B a^2 \omega}{2\sqrt{LC}} \text{ peak emf}$$

Since the circuit is in resonance,

$$|Z| = R \quad \Rightarrow \quad i_0 = \frac{\pi B a^2 \omega}{2R\sqrt{LC}} \text{ peak current}$$

$$i_{\text{rms}} = \frac{i_0}{\sqrt{2}} \quad \Rightarrow \quad i_{\text{rms}} = \frac{\pi B a^2 \omega}{2R\sqrt{2LC}}$$


$$U_C = \frac{1}{2} C V_0^2 \rightarrow \text{max. energy}, \quad V_0 \rightarrow \text{peak voltage}$$

$$V_0 = i_0 X_C = \frac{i_0}{C\omega} = \frac{i_0 \sqrt{LC}}{C}$$

$$U_C = \frac{1}{2} C \times \frac{\pi^2 B^2 a^4 \omega^2}{4R^2 C^2} = \frac{\pi^2 B^2 a^4 \omega^2}{8R^2 C}$$

$$P_{\text{Ext}} = P_{\text{Dissipated}} = \varepsilon_0 i_0 = \frac{\pi B a^2 \omega}{2\sqrt{LC}} \times \frac{\pi B a^2 \omega}{2R\sqrt{LC}}, \quad P_{\text{Ext}} = \frac{\pi^2 B^2 a^4 \omega^2}{4LCR}$$

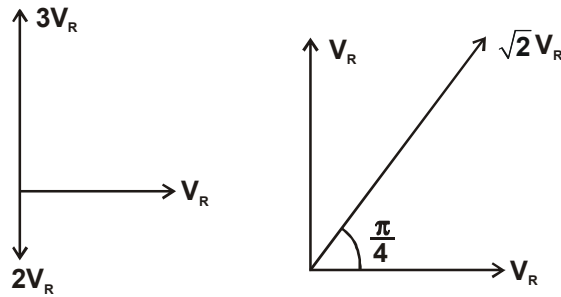17. V_R, V_L, V_C are r.m.s voltage across the R, L & C respectively



$$\theta = \frac{\pi}{4}$$

$$\text{P.F.} = \cos \theta = \frac{1}{\sqrt{2}}$$

$$\sqrt{2} V_R = 220$$

$$V_R = \frac{220}{\sqrt{2}} = 156 \text{ V}$$

18. Let N be the number of fringes within the length x , then we have,

$$\beta N = x \Rightarrow \frac{D\lambda}{d} N = x \Rightarrow N = \frac{xd}{\lambda D}$$

At any time t

$$N = \frac{x}{\lambda D} (d + vt)$$

$$\frac{dN}{dt} = \frac{xv}{\lambda D}$$

19. Changing magnetic field (at switching off B_0 to zero) induce electric field in such a way to restore the upward flux, hence anticlockwise (E) as seen from above.

$$\int \vec{E} \cdot d\vec{l} = -\frac{d\phi}{dt} = -\pi a^2 \frac{dB}{dt} = \int E dl$$

There is force on small element dQ of ring, tangentially

Now this force produces torque about axis of ring to rotate in anticlockwise sense, so,

$$\tau = \int dQE \times b = \int \lambda dl E b = \lambda b \int E dl = \lambda b \pi a^2 \frac{dB}{dt}$$

so Impulse of torque

$$\int \tau dt = \lambda b \pi a^2 \int_{B_0}^0 dB = \int \tau dt = \lambda b \pi a^2 B_0$$


$$L_f - L_i = \Delta L = \int \tau dt = \lambda b \pi a^2 B_0 = I\omega \quad (\text{in magnitude})$$

It is independent of time taken

$$I\omega_f - I\omega_i = \lambda b \pi a^2 B_0$$

Where I is moment of inertia
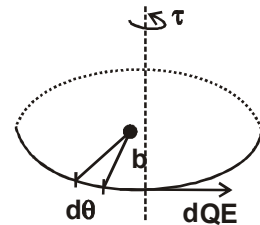
$$\text{So, } \omega_f = \frac{\lambda b \pi a^2 B_0}{mR^2}$$



20. Because both inductors are in parallel

$$\therefore L_1 I_1 = L_2 I_2$$

$$\frac{U_1}{U_2} = \frac{\frac{1}{2} L_1 I_1 I_1}{\frac{1}{2} L_2 I_2 I_2} = \frac{I_1}{I_2} = \frac{L_2}{L_1}$$

21. The path difference

$$\Delta x = (\mu_A - 1)t_A - (\mu_B - 1)t_B$$

$$\Rightarrow \Delta x = \mu_A t_A - t_A - \mu_B t_B + t_B$$

$$\Rightarrow \Delta x = t_B - t_A$$

$$\text{if } t_B = t_A \Rightarrow \Delta x = 0$$

\Rightarrow no shift

$$\text{if } t_B > t_A \text{ or } t_B < t_A$$

$$\Delta x \neq 0$$

\Rightarrow central maxima may shift towards A or B.

22. For $S_1 S_2 = 2.5\lambda$, max path different = 2.5λ
min path different = 0

Between 2.5λ and 0 lie 2λ and $\lambda \Rightarrow$ two circular bright fringes

$$n_1 = 2$$

For $S_1 S_2 = 5.7\lambda$, max. path different = 5.7λ
min path different = 0

Between 5.7λ and 0 lie 5λ , 4λ , 3λ , 2λ , $\lambda \Rightarrow$ Five circular bright fringes.

$$\Rightarrow n_2 = 5$$

$$\therefore n_2 - n_1 = 5 - 2 = 3$$

23.
$$\varepsilon = -\frac{\Delta\phi}{\Delta t} = -\frac{(\phi_2 - \phi_1)}{\Delta t}$$

$$= \frac{\phi_1 - \phi_2}{\Delta t}$$

$$= \frac{BA - 0}{\Delta t} = \frac{0.5 \times \pi (1 \times 10^{-2})^2}{0.5} = \pi \times 10^{-4} \text{ V}$$

24. Just after the switch is closed, there is no current through the coil and capacitor offers no resistance.

$$\text{Net Resistance} = \frac{9}{2} = 4.5 \Omega \Rightarrow i_0 = \frac{18}{4.5} = 4 \text{ A.}$$

25. For $R_1 - L$ branch

$$X_L = \omega L = 100 \times \frac{\sqrt{3}}{10} = 10\sqrt{3} \Omega, R_1 = 10 \Omega$$

$$\therefore \tan \phi = \frac{X_L}{R_1} = \sqrt{3} \quad \text{or} \quad \phi = 60^\circ$$

Hence current I_1 lags voltage by 60° .

For $R_2 - C$ branch

$$X_C = \frac{1}{\omega C} = \frac{1}{100 \times \frac{\sqrt{3}}{2} \times 10^{-3}} = \frac{20}{\sqrt{3}} \Omega$$

$$\therefore \tan \phi = \frac{X_C}{R_2} = \frac{1}{\sqrt{3}} \quad \text{or} \quad \phi = 30^\circ$$

Hence current I_2 leads voltage by 30° .

\therefore The phase difference between I_1 and I_2 is 90° .

The maximum current through $R_1 - L$ branch is

$$= \frac{V_0}{\sqrt{R_1^2 + \omega^2 L^2}} = \frac{200\sqrt{2}}{\sqrt{10^2 + (10\sqrt{3})^2}} = 10\sqrt{2} \text{ amp.}$$

Hence when current through $R_1 - L$ branch is $10\sqrt{2}$ amp., the current through $R_2 - C$ branch will be zero.


26. $P = \frac{V^2}{R}$

20V peak ac is equivalent to $\frac{20}{\sqrt{2}}$ dc

i.e. 14.14V dc power

$\frac{\text{dc power}}{\text{ac power}}$
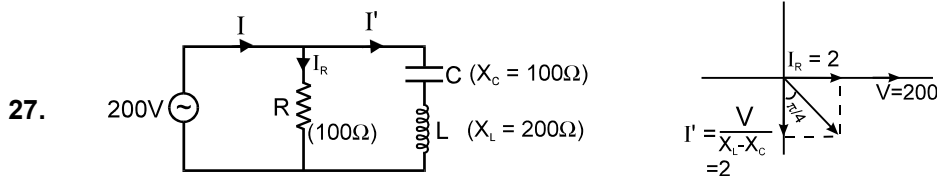
$$= \frac{\left(\frac{20^2}{R}\right)}{\left[\left(\frac{20}{\sqrt{2}}\right)^2 / R\right]} = \frac{20^2}{\left(\frac{20}{\sqrt{2}}\right)^2} = 2$$



$$I_R = \frac{V}{R} = \frac{200}{100} = 2A$$

$$I' = \frac{V}{X_L - X_C} = \frac{200}{100} = 2A$$

$$I = \sqrt{I_R^2 + I'^2} = 2\sqrt{2} \text{ Amp.}$$

29. $\frac{\lambda D_1}{d} - \frac{\lambda D_2}{d} = 3 \times 10^{-5}$

$$\lambda \times \frac{5 \times 10^{-2}}{10^{-3}} = 3 \times 10^{-5} \Rightarrow \lambda = 0.6 \times 10^{-6} = 6000 \text{ \AA.}$$

30. Shift of fringe pattern = $(\mu - 1) \frac{tD}{d}$

$$\therefore \frac{30 D (4800 \times 10^{-10})}{d} = (0.6) t \frac{D}{d}$$

$$30 \times 4800 \times 10^{-10} = 0.6$$

$$t = \frac{30 \times 4800 \times 10^{-10}}{0.6} = \frac{1.44 \times 10^{-5}}{0.6} = 24 \times 10^{-6}$$

31 to 33

Considering length of line is

$$E = \frac{\sigma}{\epsilon_0} \Rightarrow V = Eh$$


$$V = \frac{\sigma}{\epsilon_0} h = \frac{Q}{\epsilon_0 b \ell} \cdot h = c = \frac{Q}{v}$$

$$C = \frac{\epsilon_0 b \ell}{h}$$

$$\frac{C}{\ell} = \frac{\epsilon_0 b}{h}$$

$$\Rightarrow B = \frac{\mu_0 K}{2} + \frac{\mu_0 K}{2} = \mu_0 K = \frac{\mu_0 I}{b} \quad (K = \text{current per unit width})$$
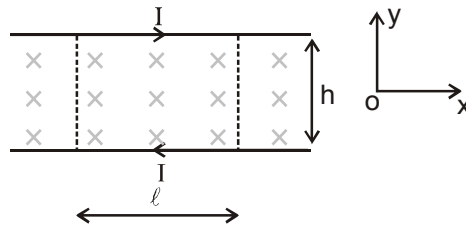
$$\vec{B} = \frac{\mu_0 I}{b} (-\hat{k})$$



Consider a rectangular surface as shown in the figure.

Now $\phi = Bh\ell$

$$\phi = \frac{\mu_0 I}{b} \cdot h \ell = LI$$

$$L = \frac{\mu_0 h \ell}{b}$$

$$\frac{L}{\ell} = \frac{\mu_0 h}{b} \quad \text{But}$$

$$c = \frac{1}{\sqrt{\mu_0 \epsilon_0}}$$

$$c^2 = \frac{1}{\mu_0 \epsilon_0}$$

$$\mu_0 = \frac{1}{\epsilon_0 c^2}$$

$$\frac{L}{\ell} = \frac{h}{\epsilon_0 c^2 b}$$

34 to 36

The fan is operating at 200 V, consuming 1000 W, then $I = \frac{1000}{200} = 5A$

But as coil resistance is 1Ω then power dissipated by internal resistance heat is $P_1 = I^2R = 25W$
If V is net emf across coil then

$$\frac{V^2}{R} = 25 W \quad V = 5 \text{ volt}$$

Net emf = source emf – back emf

$$V = V_s - e \quad \Rightarrow \quad e = 195 V$$

The work done $P_2 = 1000 - 25 = 975 W$.

37. Explanation :



For $r < R$

$$\oint E dl = A \frac{dB}{dt}$$

$$E 2\pi r = (\pi r^2) \alpha$$

$$E = \frac{r\alpha}{2} \text{ or } E \propto r$$

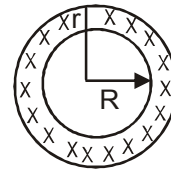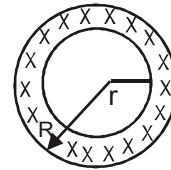So, E - r graph is a straight line passing through origin.



At $r = R$

$$E = \frac{R\alpha}{2}$$

For $r > R$

$$E 2\pi r = (\pi R^2) \alpha$$

Hence, choice (a) is correct and choices (b), (c) and (d) are wrong.

38. Explanation :

Perpendicular distance between BC and centre O is 10 cm. Component of induced electric field along

$$\text{the rod} = \frac{d}{2} \frac{dB}{dt}$$

Where d = Perpendicular distance from centre to the rod.

Hence, potential difference between the ends of rod

$$v = EI = l \cdot \frac{d}{2} \frac{dB}{dt}$$

$$= \frac{10}{2} \times 10^{-2} \times 20 \times 10^{-2} \times 2 = 20 \text{ mV}$$

Hence, choice (b) is correct and choices (a), (c) and (d) are wrong.

39. Explanation :

Perpendicular distance between CD and O is 20 cm.

Therefore, induced emf in CD

$$= \frac{d}{2} \frac{dB}{dt} = \frac{20}{2} \times 10^{-2} \times 20 \times 10^{-2} \times 2$$


$$= 40 \text{ mV}$$

40. Path difference,

$$\Delta x = n_1 SS_2 + n_2 S_2 P - \left[(n_1 SS_1 + n_2 S_1 P) - \int_0^t (n_3 - n_2) dx \right]$$

$$= n_1 (SS_2 - SS_1) + n_2 (S_2 P - S_1 P) - \int_0^t n_3 dx + n_2 t$$

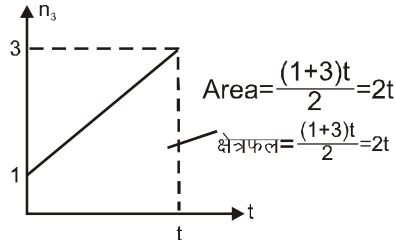In order to get central maxima at centre of screen –



$$0 = \frac{2 \times (1 \times 10^{-3})^2}{2 \times 1} + 0 - 2t + \frac{3t}{2}$$

$$0.5 t = 1 \mu\text{m}.$$

$$t = 2 \mu\text{m}.$$

41. From previous equation :

$$0 = 1 \mu\text{m} + \frac{3yd}{2D} - 0.5 t$$

$$\frac{3 yd}{2 D} = -0.5 \mu\text{m}$$

$$y = - \left(\frac{10^{-6}}{3} \right) \left(\frac{1\text{m}}{1 \times 10^{-3}} \right) = \frac{10^{-3}}{3} = \frac{-1}{3} \text{ mm, below centre.}$$

$$42. \beta = \frac{\lambda D}{n_2 d} = \frac{3000 \times 10^{-10} \times 1 \times 2}{3 \times 1 \times 10^{-3}} = 2 \times 10^{-4} \text{ m} = 0.2 \text{ mm}.$$

44. **Explanation :**

Time varying magnetic field produced electric field known as induced electric field.

So (P) \rightarrow (4)

For $r < R$


$$\oint E \cdot dl = - \frac{d\Phi}{dt}$$

$$E 2\pi r = - \pi r^2 \frac{dB}{dt}$$

$$E = - \frac{r}{2} \frac{dB}{dt}$$

So (Q) \rightarrow (2)

For $r > R$.

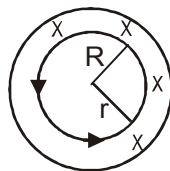


$$E 2\pi r = - \pi R^2 \frac{dB}{dt} \text{ ss, } E = - \frac{R^2}{2r} \frac{dB}{dt}$$


So (R) \rightarrow (3)

If rod is placed along the diameter of magnetic field, then electric field is perpendicular to length of rod.


45. power = i^2R graph of 'i' vs f is :

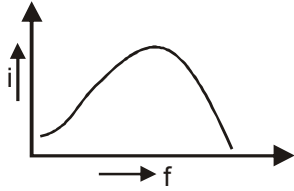

From data, the possibilities are

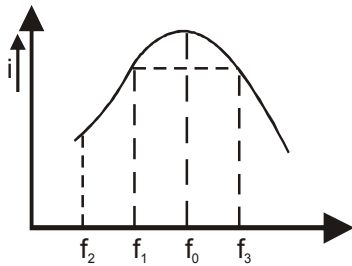

or

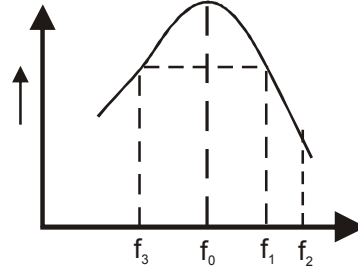

f_0 is resonant frequency \Rightarrow means same as circuit being resistive.

The circuit is capacitive when $f < f_0$ and inductive when $f > f_0$

Power at f_1 and f_3 same $\Rightarrow i$ same $\Rightarrow z$ same

$$\Rightarrow 2\pi f_1 L - \frac{1}{2\pi f_1 C} = \frac{1}{2\pi f_3 C} - 2\pi f_3 L$$

$$\Rightarrow 2\pi L (f_1 + f_3) = \frac{1}{2\pi C} \left(\frac{1}{f_1} + \frac{1}{f_3} \right)$$

$$\Rightarrow f_1 f_3 = \frac{1}{4\pi^2 LC} \Rightarrow \sqrt{f_1 f_3} = \frac{1}{2\pi\sqrt{LC}} = \frac{\omega_0}{2\pi}$$

$$AM > GM \Rightarrow \frac{f_1 + f_3}{2} > f_0$$

$$\Rightarrow \text{Inductive at frequency} = \frac{f_1 + f_3}{2}.$$